
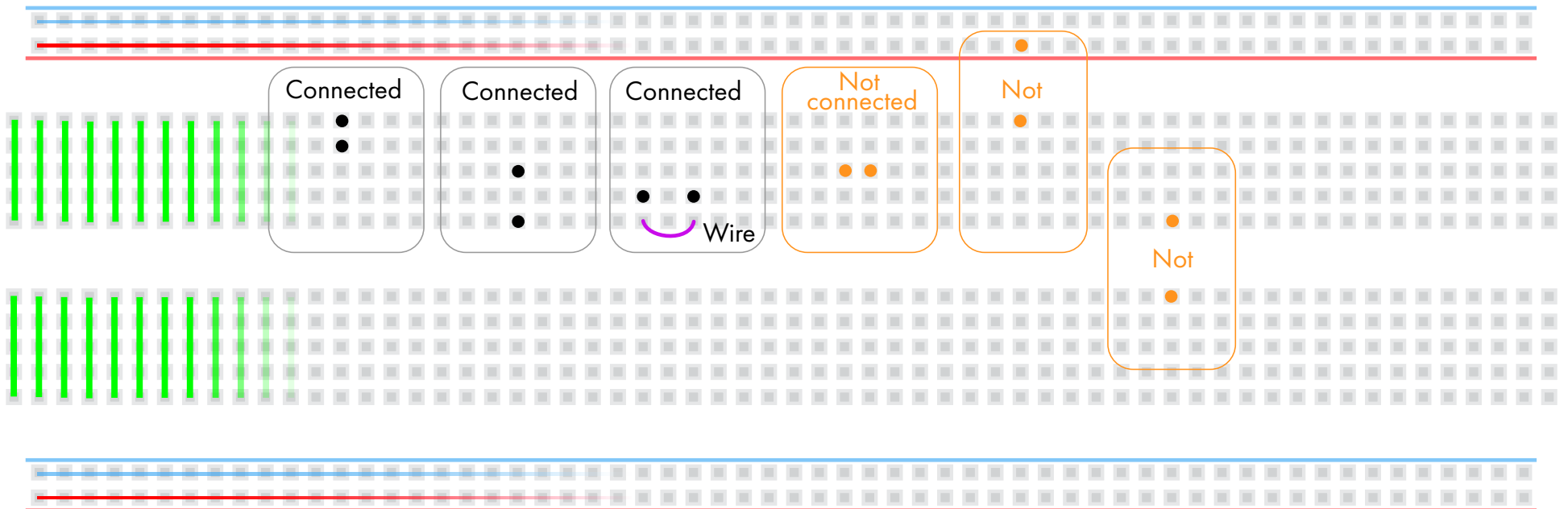



Getting to know the breadboard

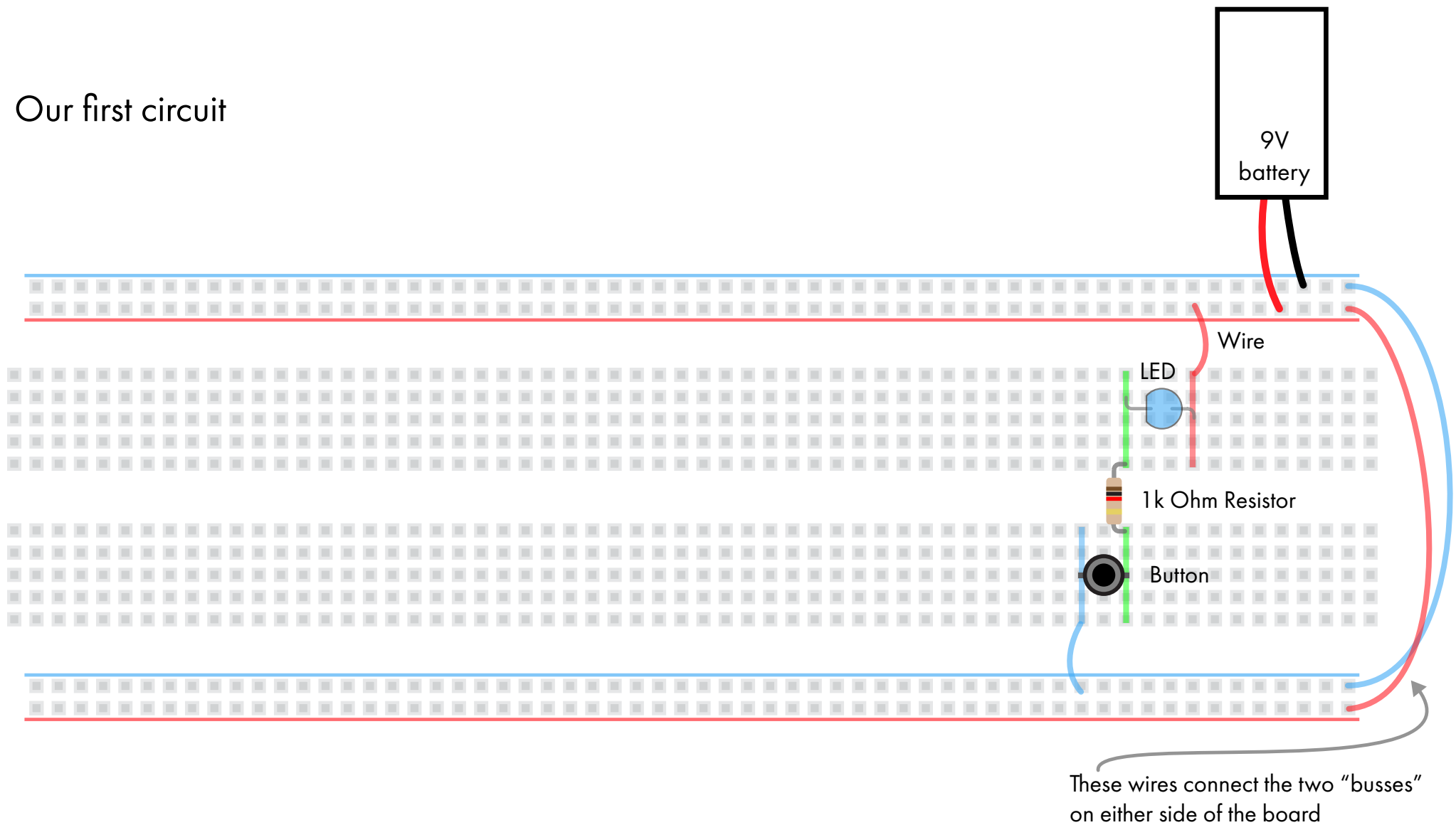


Our first circuit




Two LEDs

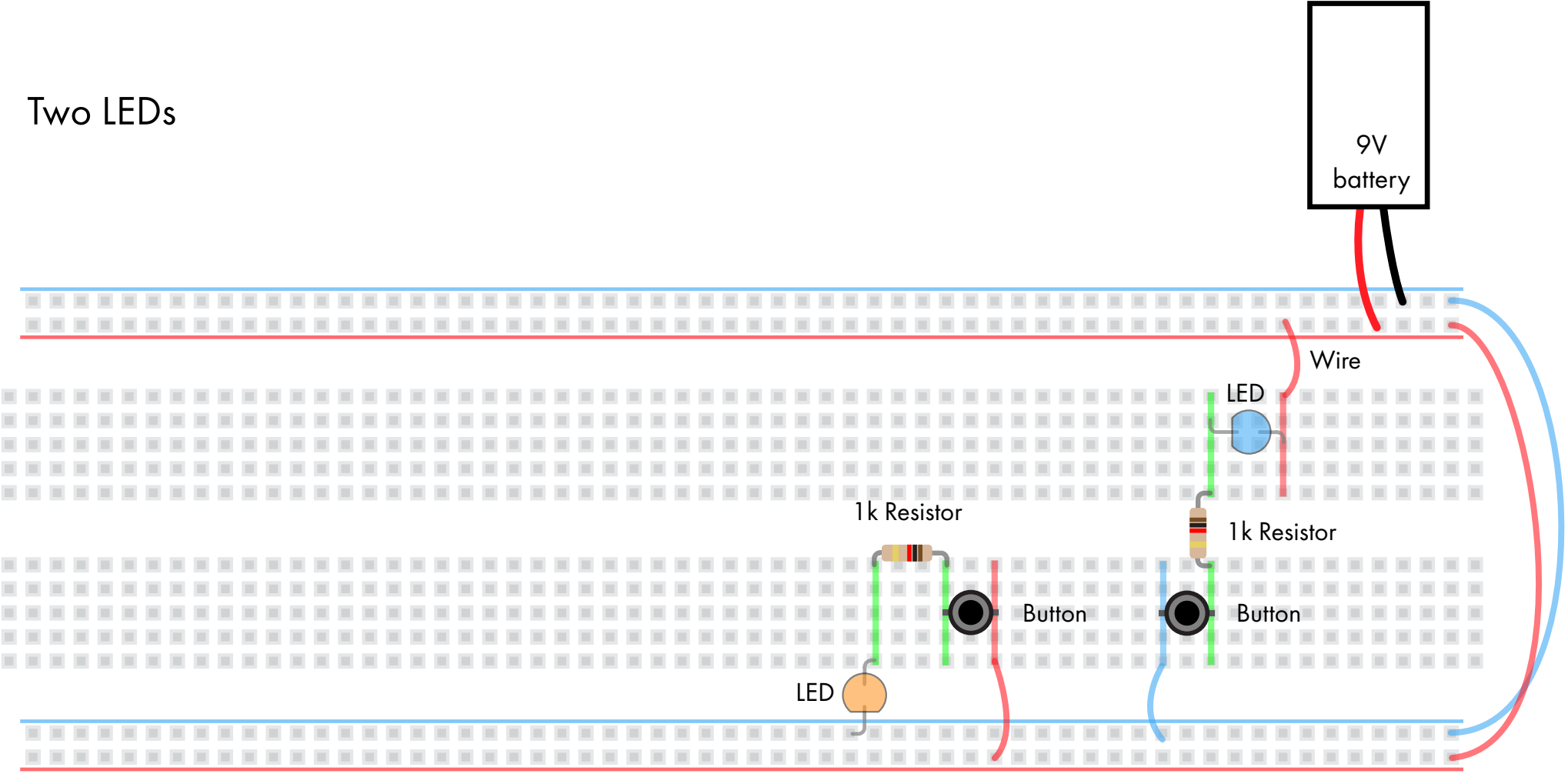

Arduino / Teensy

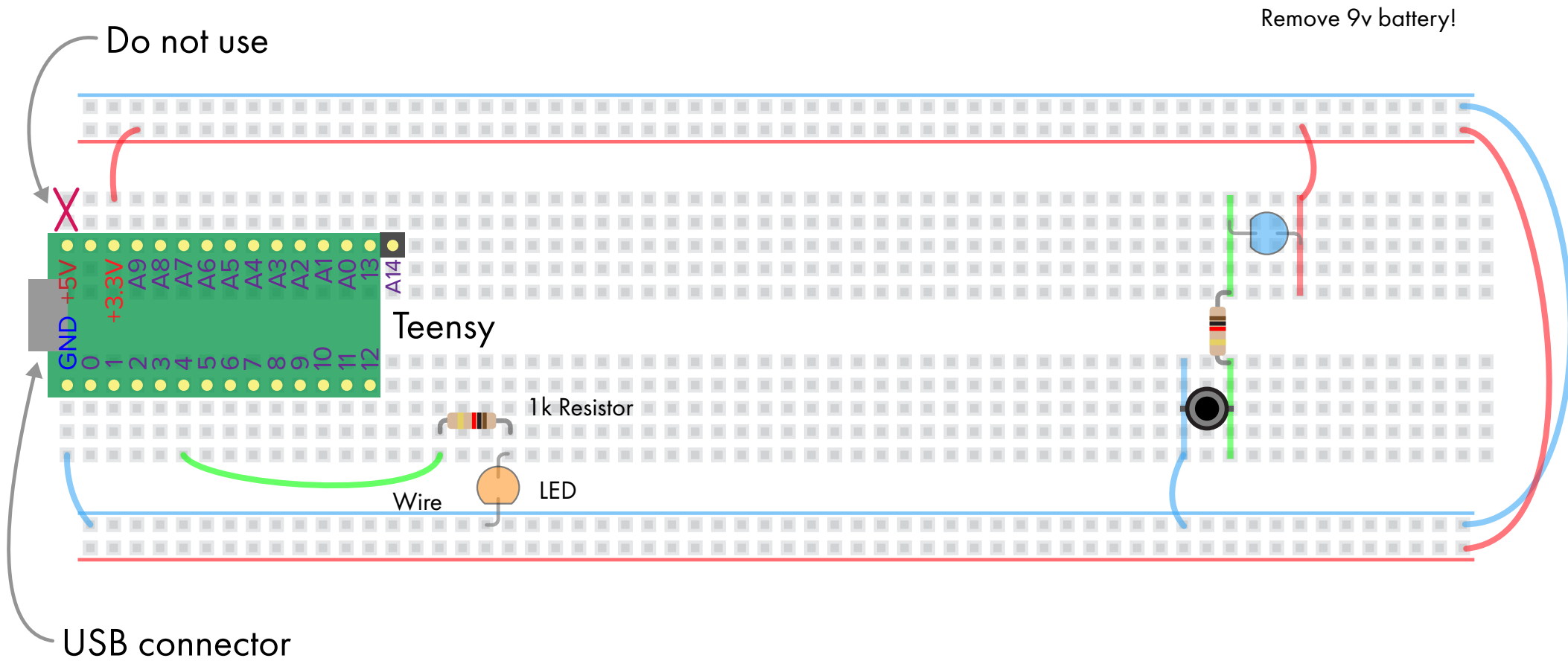

Code controlling two LEDs

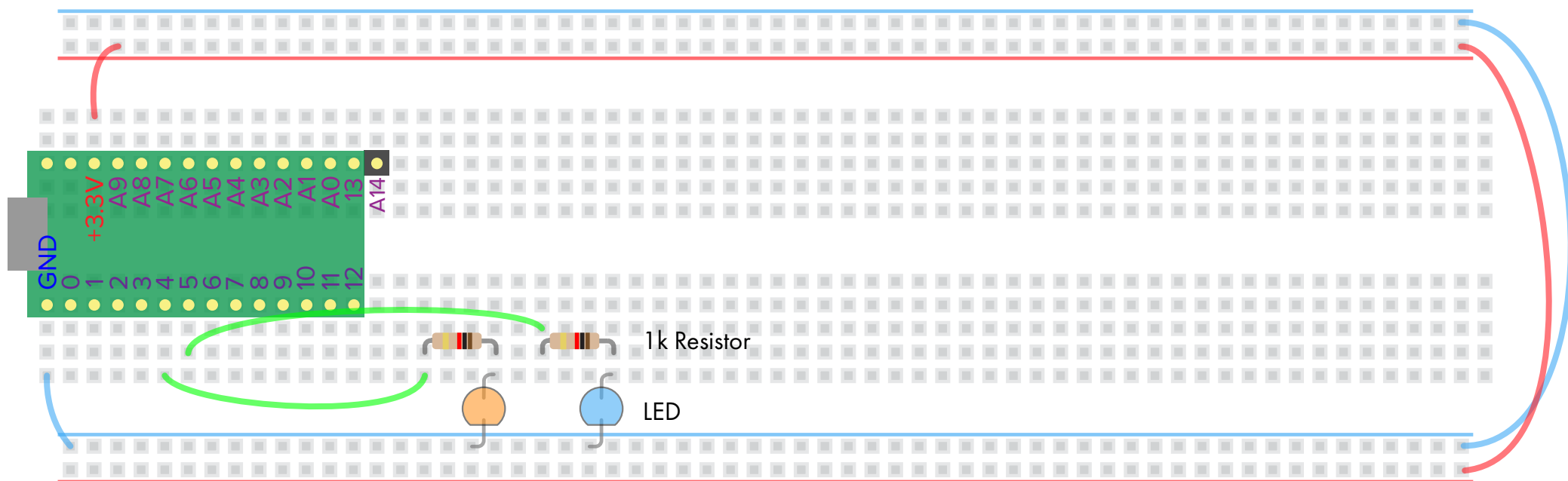

Analog Read

